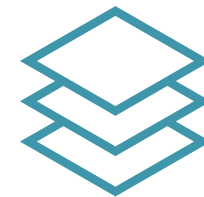


Bab 5 Prategangan BJT



Memahami karakteristik dan mampu menganalisis rangkaian dengan transistor



Prategangan DC

PRATEGANGAN DC

Prategangan DC

Tegangan-tegangan transistor NPN :

	$V_{CE \text{ sat}}$	$V_{BE \text{ sat}}$	$V_{BE \text{ aktif}}$
Si	0,2	0,8	0,7
Ge	0,1	0,3	0,2


$$V_{BE} = 0,7V$$

$$I_E = (\beta + 1)I_B \approx I_C$$



$$I_C = \beta I_B$$


Prosedur Analisis Prategangan DC:

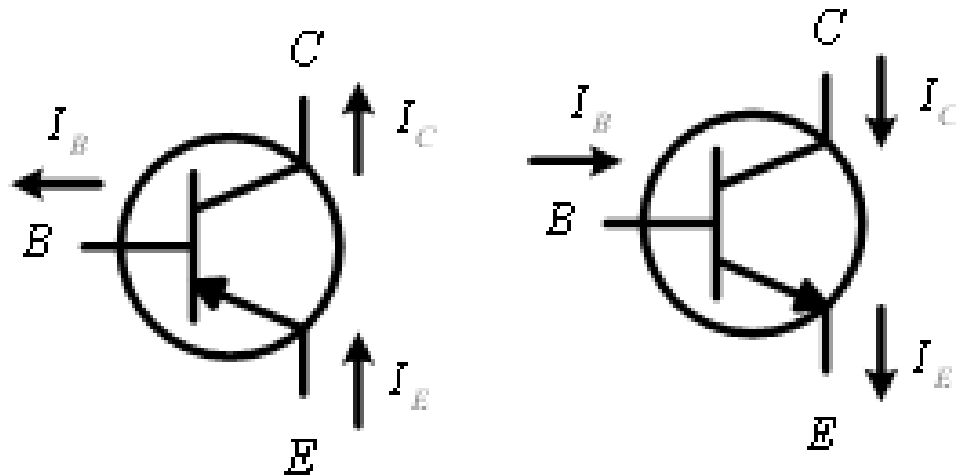- Input ac diganti dengan tahanan dalamnya (prinsip superposisi)
- Komponen kapasitor dibuat open circuit
- Buat arus yang sesuai dengan jenis transistor





Rangkaian Prategangan Tetap

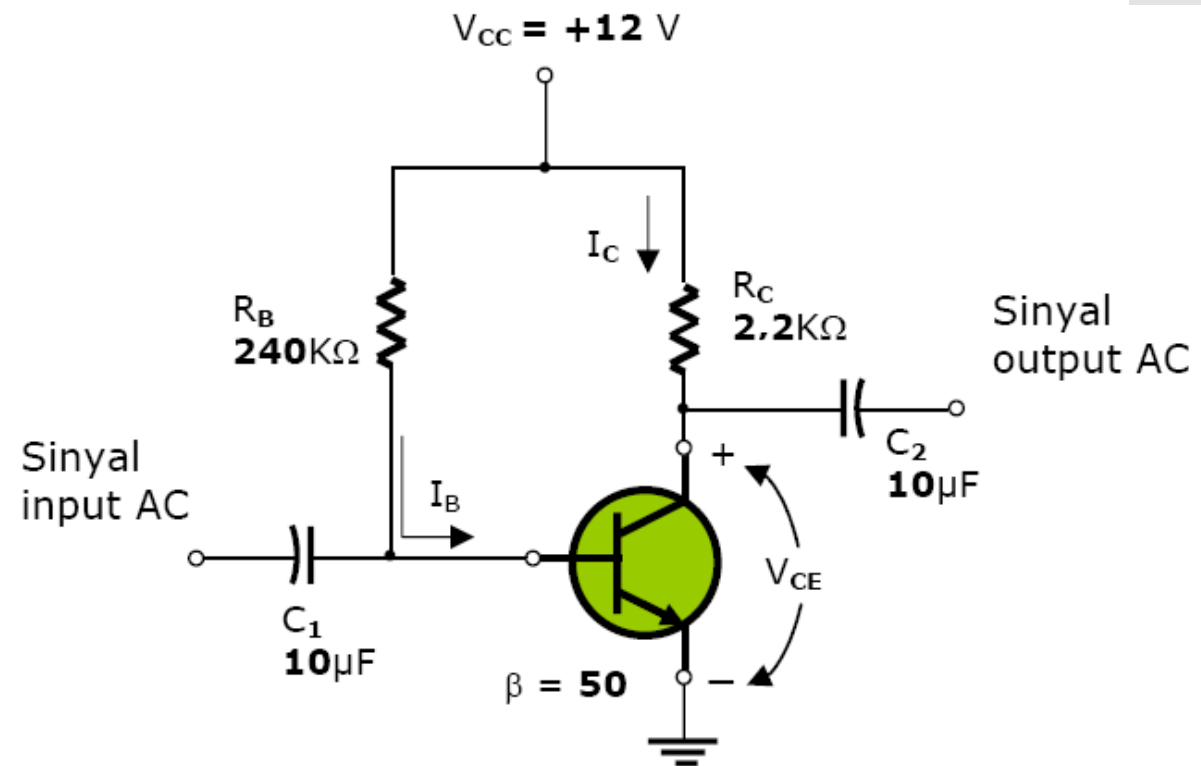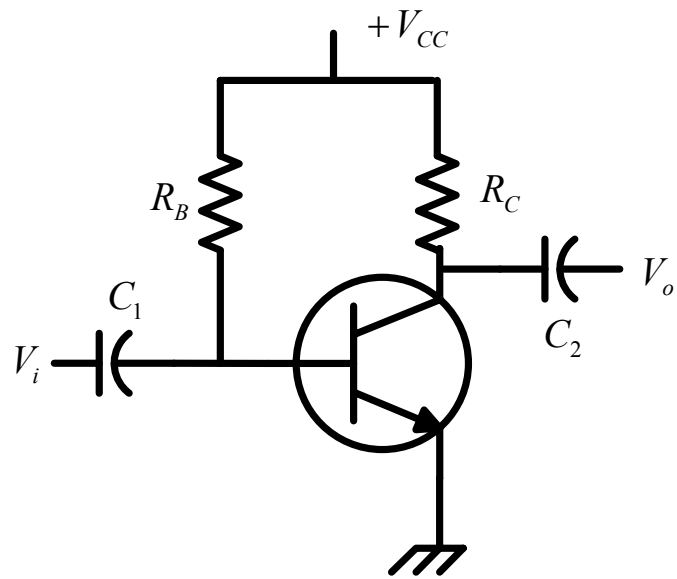


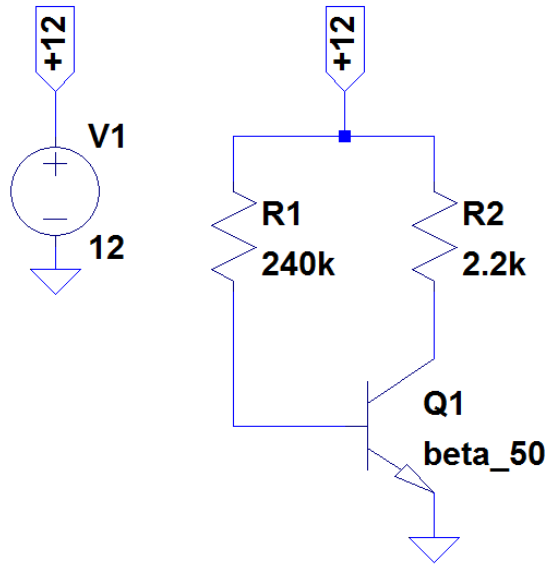

```
--- Operating Point ---  
V(+12) :      12          voltage  
V(n002) :      0.796156   voltage  
V(n001) :      6.8649     voltage  
Ic(Q1) :      0.00233416  device_current  
Ib(Q1) :      4.66833e-005 device_current  
Ie(Q1) :      -0.00238085 device_current  
I(R2) :      0.00233413  device_current  
I(R1) :      4.66827e-005 device_current  
I(V1) :      -0.00238082 device_current
```

Rangkaian Prategangan Penstabil Emitor

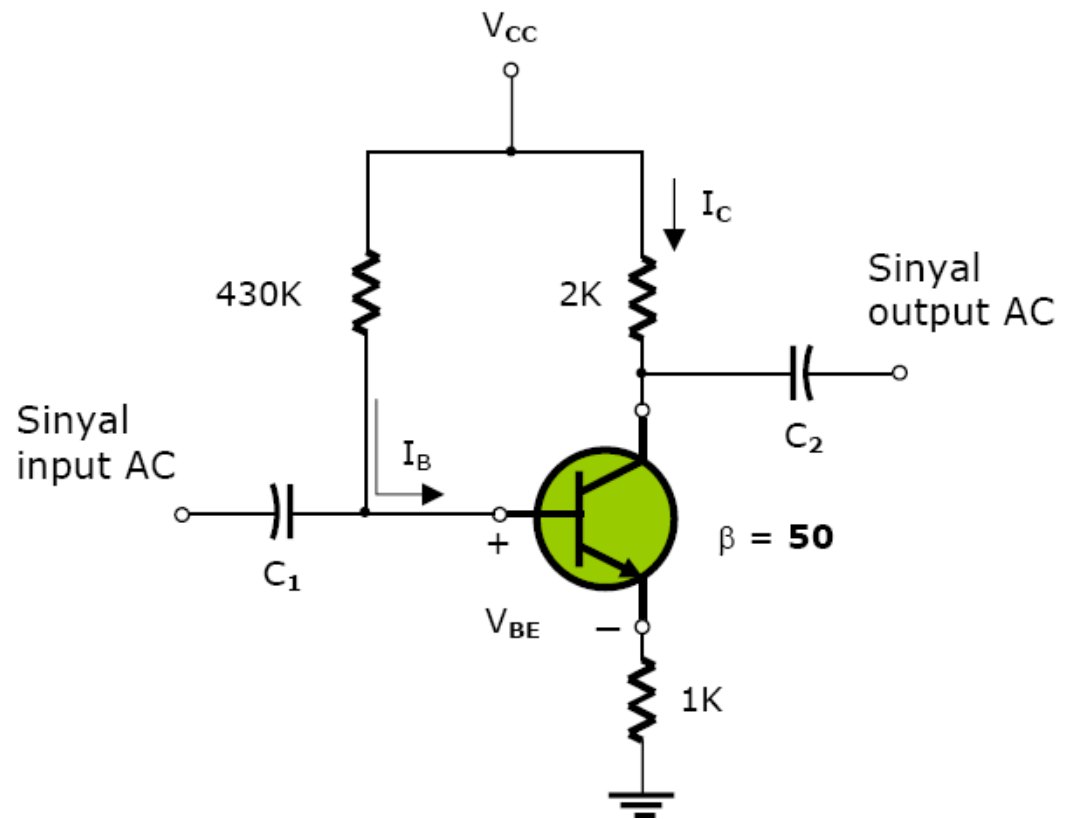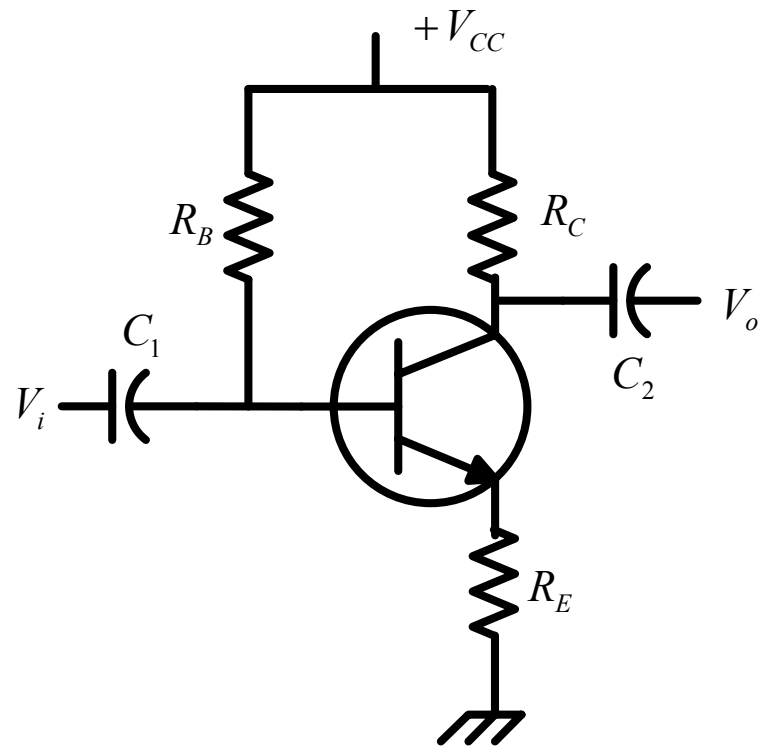


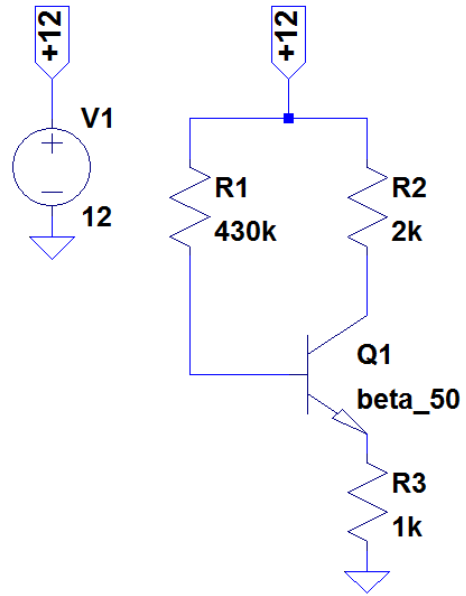



```

--- Operating Point ---
V(+12) :      12          voltage
V(n002) :      1.96805   voltage
V(n001) :      9.66699   voltage
V(n003) :      1.18984   voltage
Ic(Q1) :      0.00116651 device_current
Ib(Q1) :      2.33301e-005 device_current
Ie(Q1) :      -0.00118984 device_current
I(R3) :      0.00118984  device_current
I(R2) :      0.00116651  device_current
I(R1) :      2.33301e-005 device_current
I(V1) :      -0.00118984 device_current

```

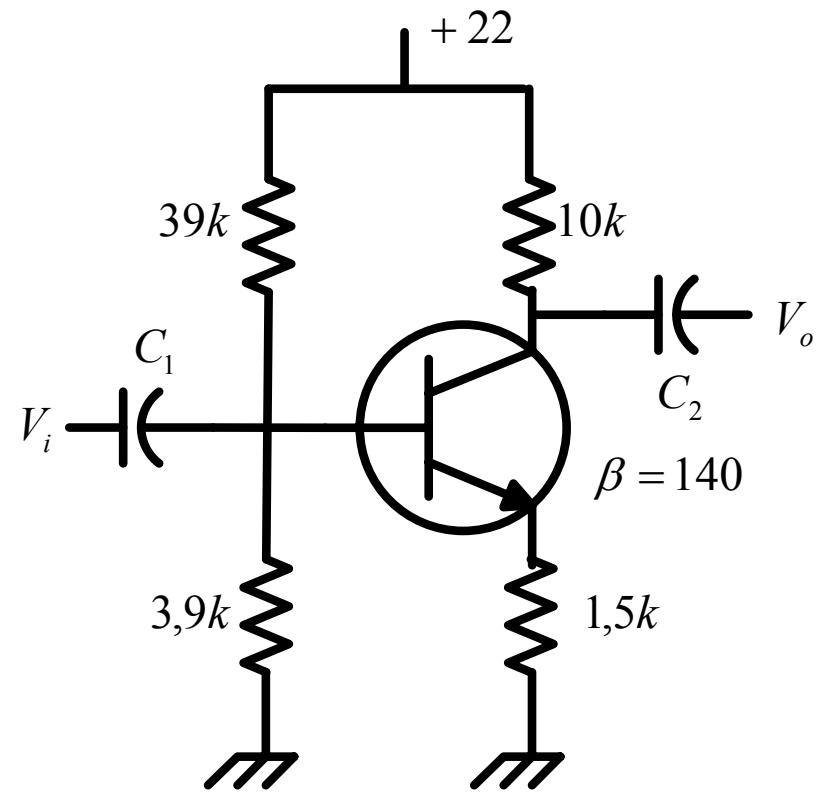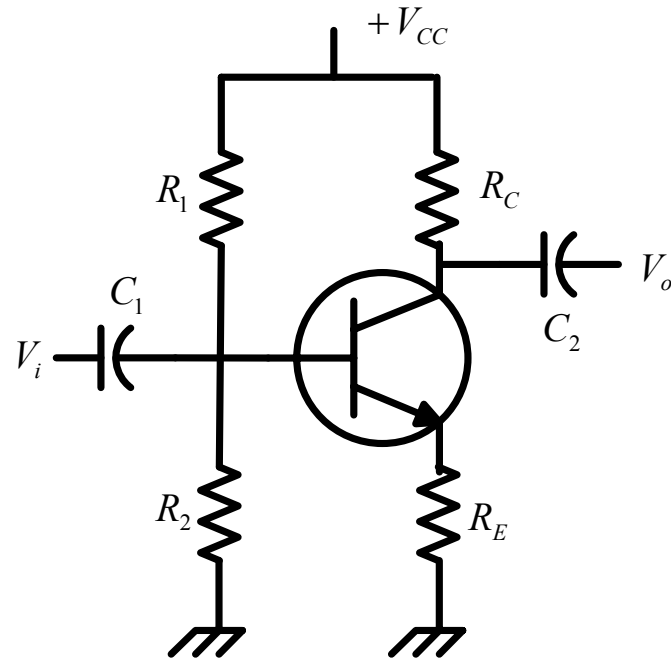
Rangkaian Prategangan Sendiri/ Pembagi Tegangan





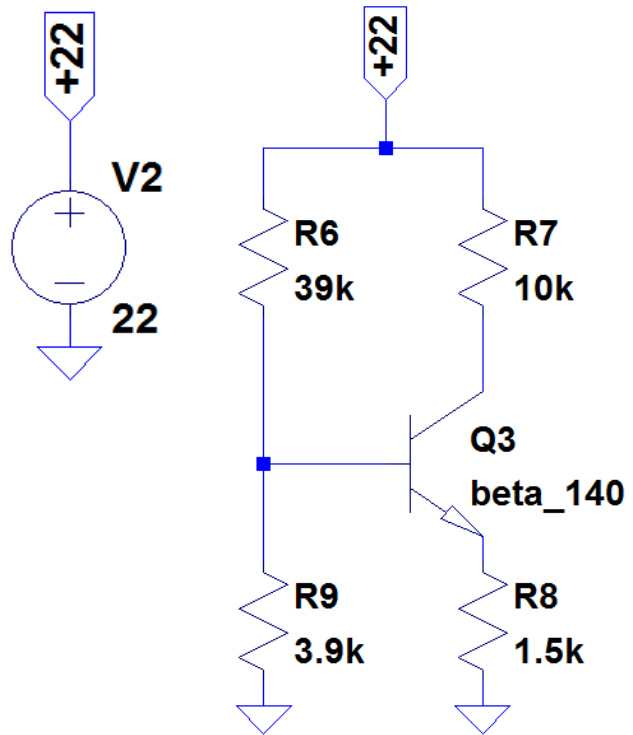


--- Operating Point ---

V(+22):	22	voltage
V(n002):	1.9797	voltage
V(n001):	13.9827	voltage
V(n003):	1.21118	voltage
Ic(Q1):	0.00080175	device_current
Ib(Q1):	5.72678e-006	device_current
Ie(Q1):	-0.000807477	device_current
I(R4):	0.000507615	device_current
I(R3):	0.000807454	device_current
I(R2):	0.000801727	device_current
I(R1):	0.000513341	device_current
I(V1):	-0.00131507	device_current

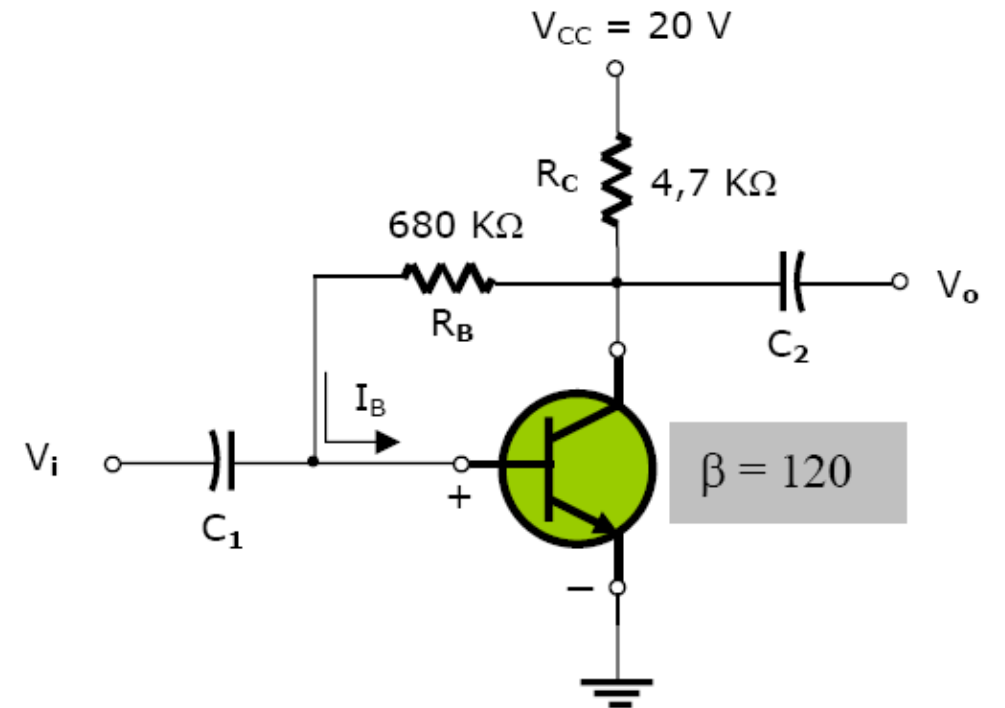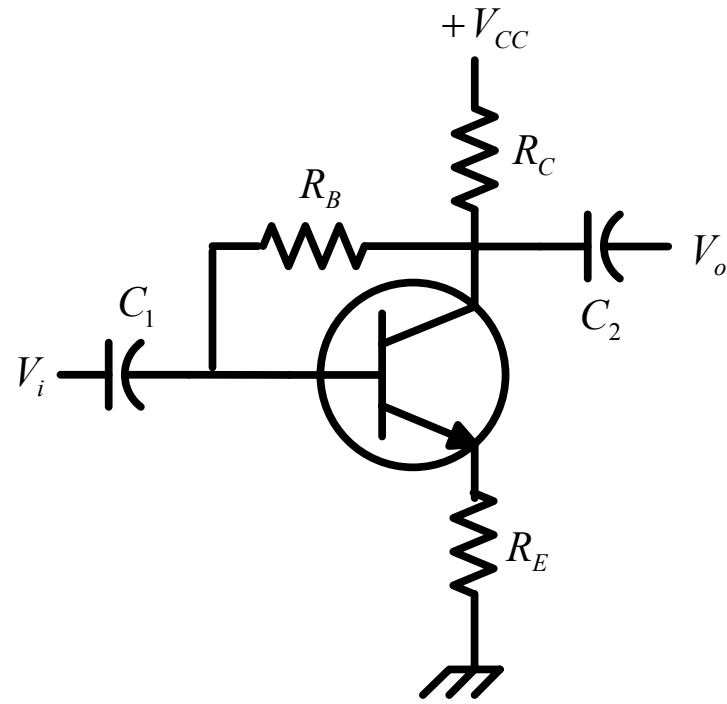
Prategangan DC Collector ke Basis / Umpan Balik




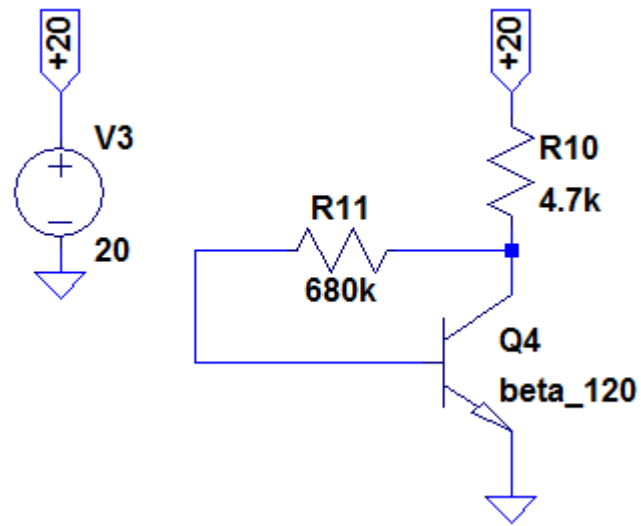

--- Operating Point ---

V(+20) :	20	voltage
V(n002) :	11.2512	voltage
V(n001) :	0.790088	voltage
Ic(Q1) :	0.00184607	device_current
Ib(Q1) :	1.53839e-005	device_current
Ie(Q1) :	-0.00186146	device_current
I(R2) :	1.53839e-005	device_current
I(R1) :	0.00186146	device_current
I(V1) :	-0.00186146	device_current

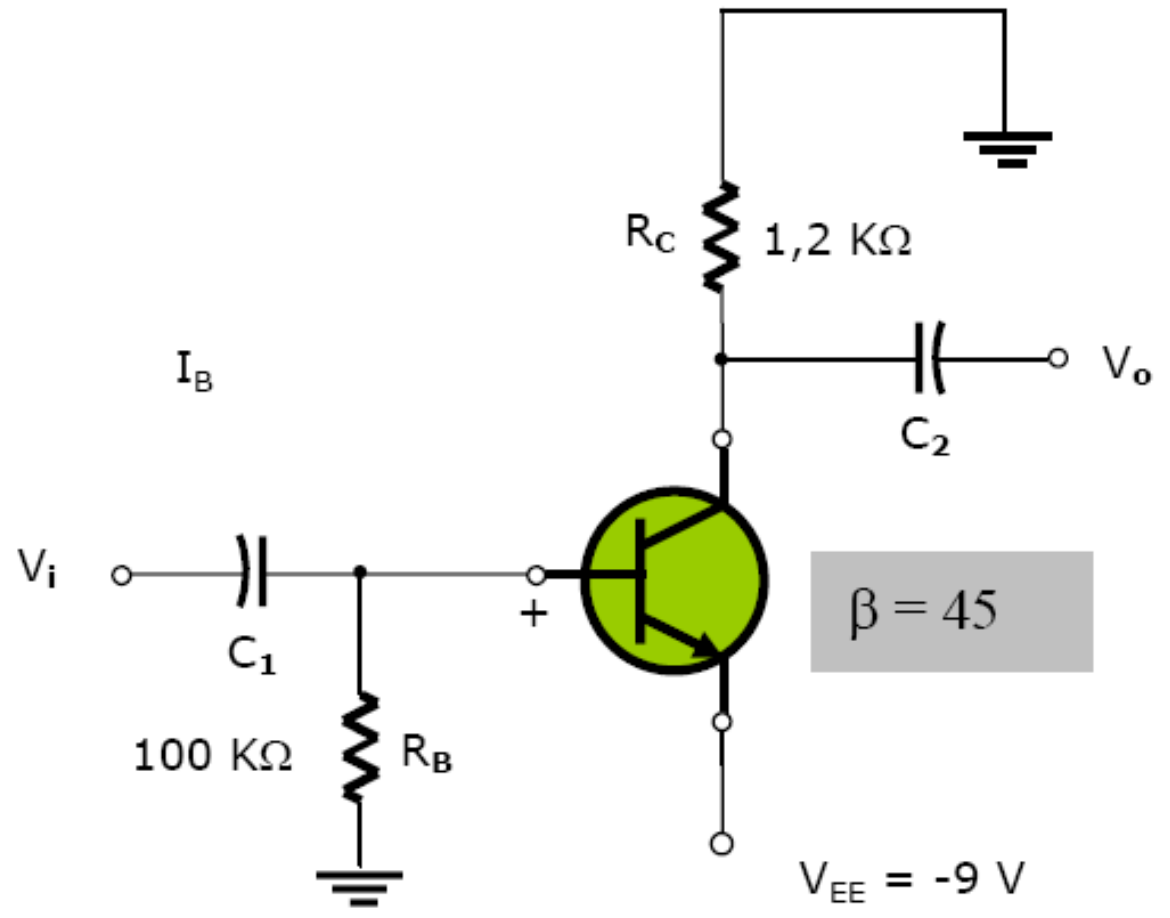


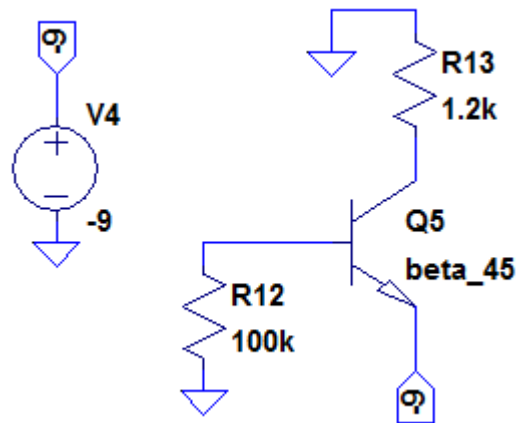


```

--- Operating Point ---
V(-9) :          -9          voltage
V(n002) :        -8.19202    voltage
V(n001) :        -4.42369    voltage
Ic(Q1) :         0.00368641   device_current
Ib(Q1) :         8.19202e-005 device_current
Ie(Q1) :        -0.00376833   device_current
I(R2) :          0.00368641   device_current
I(R1) :        -8.19202e-005 device_current
I(V1) :          0.00376833   device_current





```





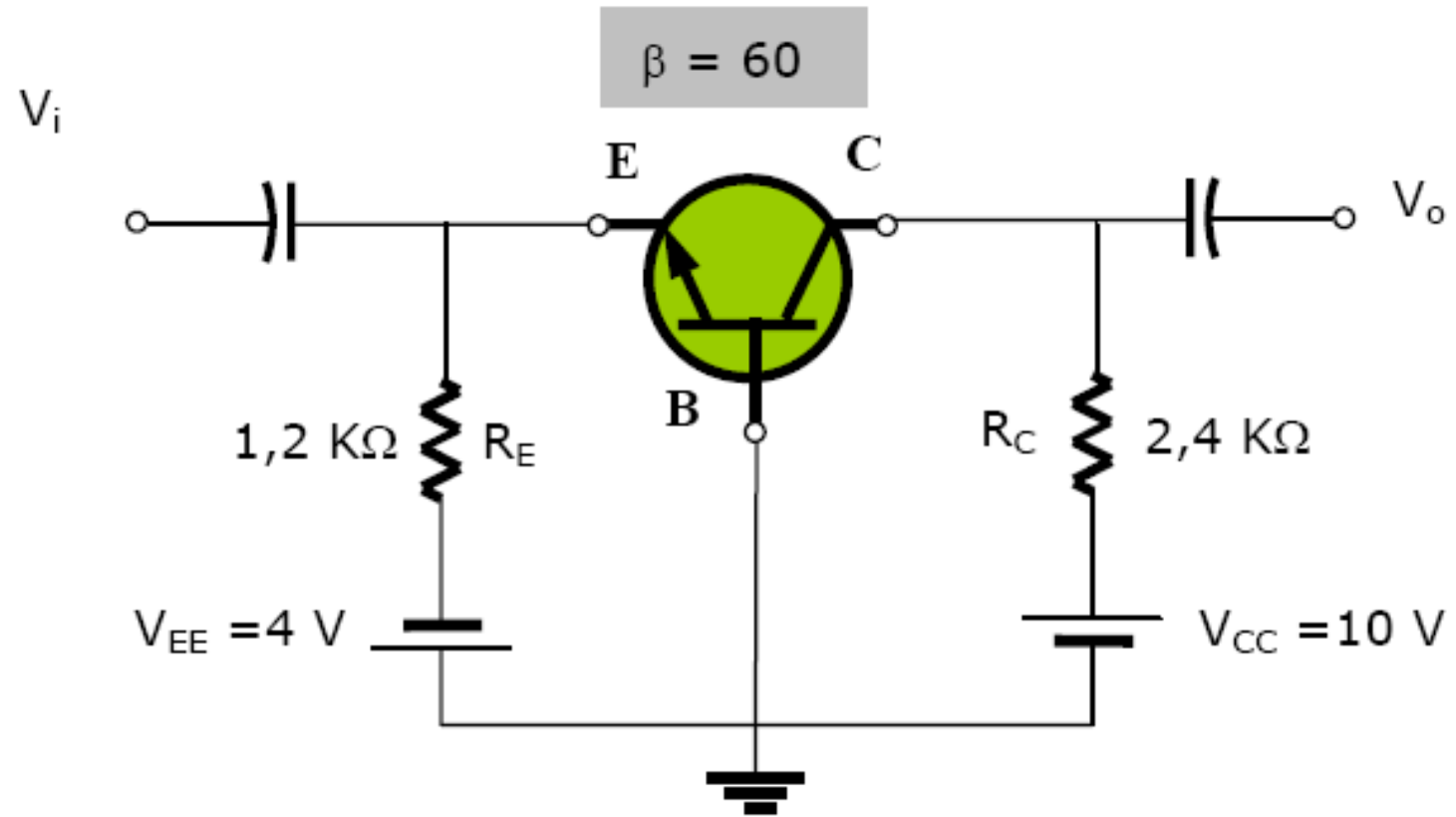


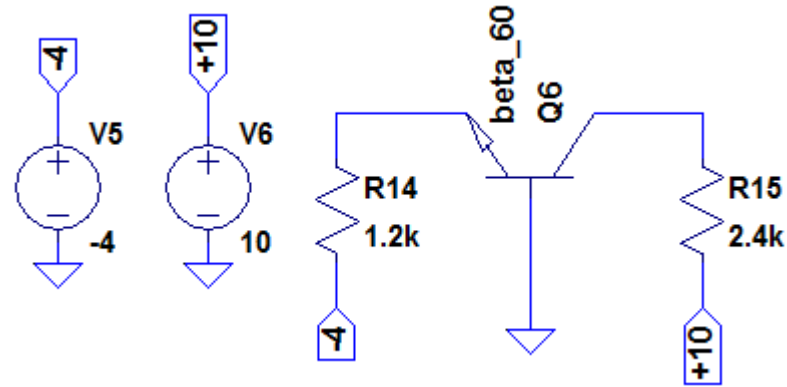


--- Operating Point ---

V(n002) :	3.7033	voltage
V(n001) :	-0.79918	voltage
V(-4) :	-4	voltage
V(+10) :	10	voltage
Ic(Q1) :	0.00262363	device_current
Ib(Q1) :	4.37272e-005	device_current
Ie(Q1) :	-0.00266736	device_current
I(R2) :	-0.00262362	device_current
I(R1) :	0.00266735	device_current
I(V2) :	-0.00262362	device_current
I(V1) :	0.00266735	device_current

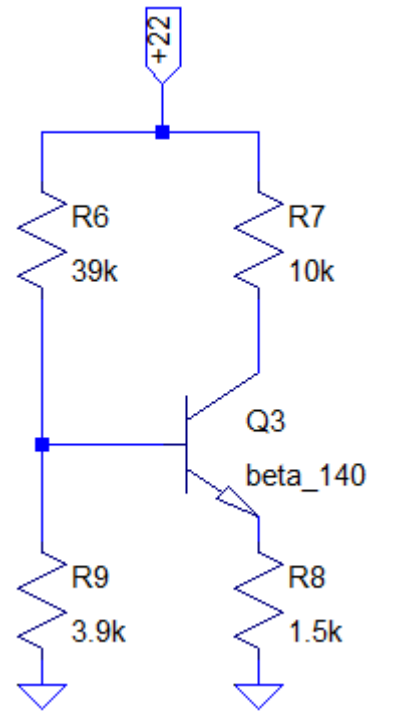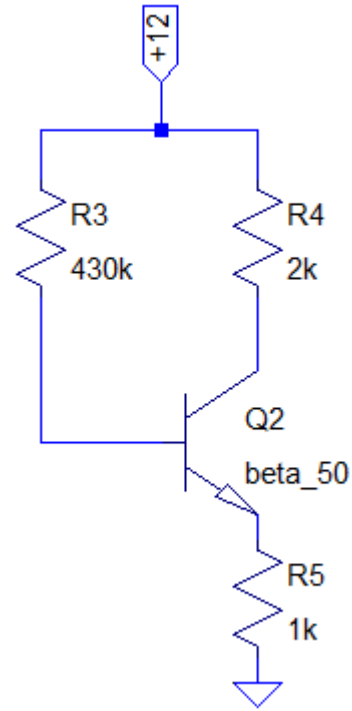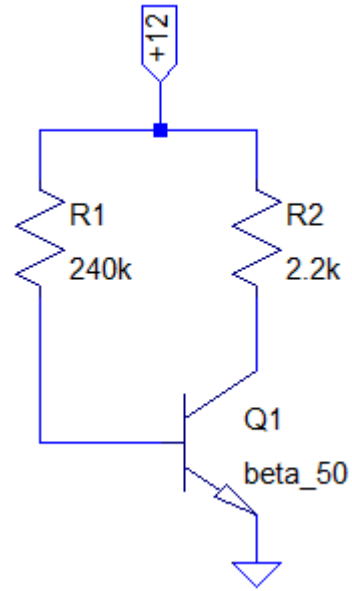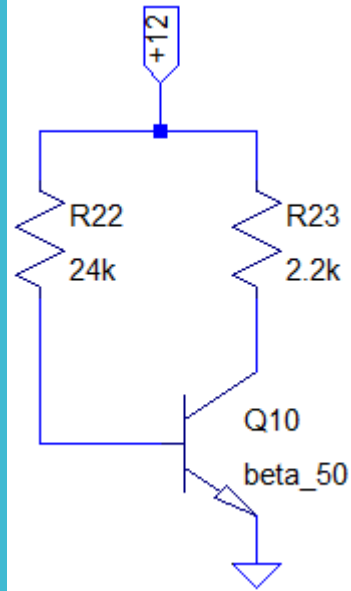

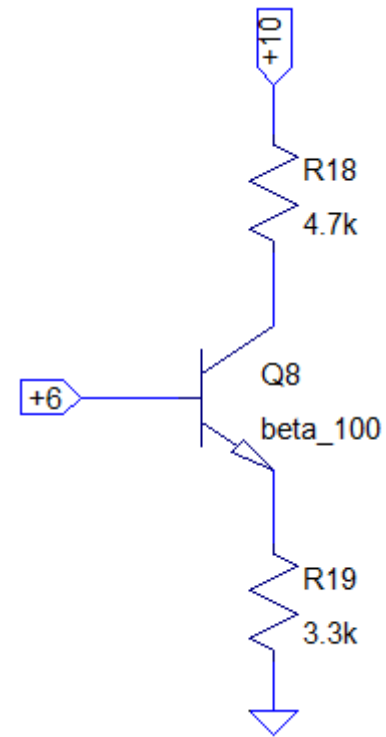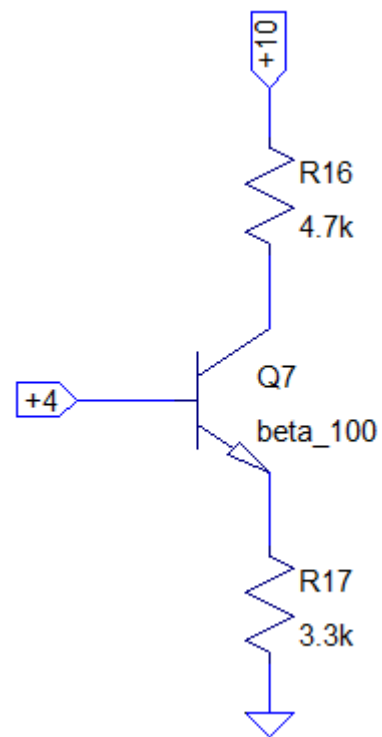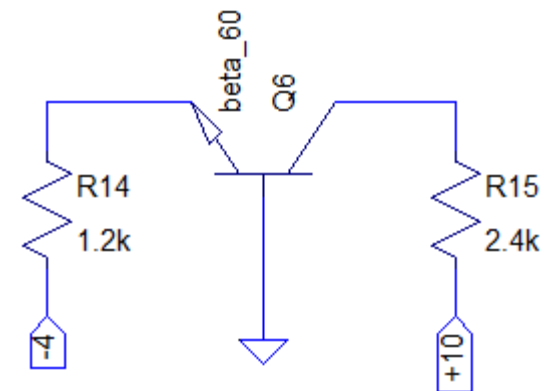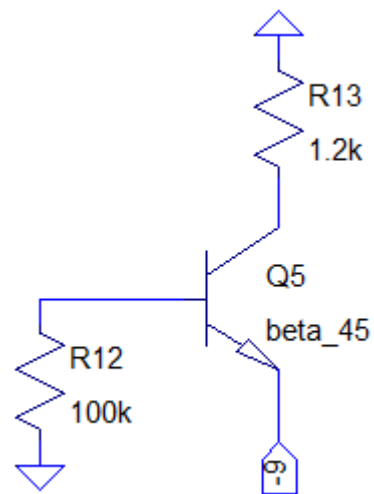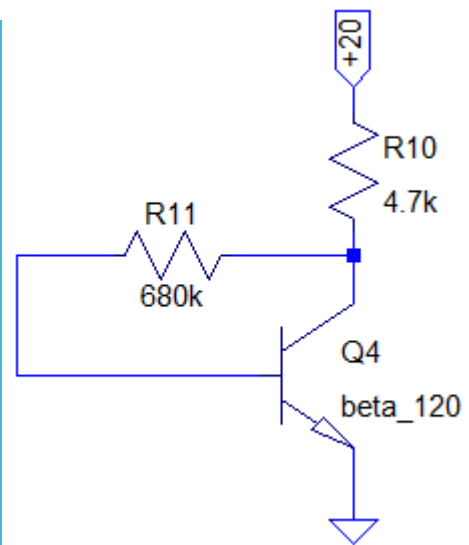


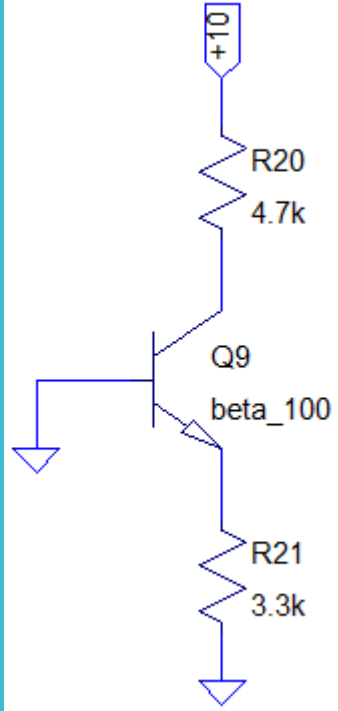

Q9
beta_100

R21
3.3k


R20
4.7k

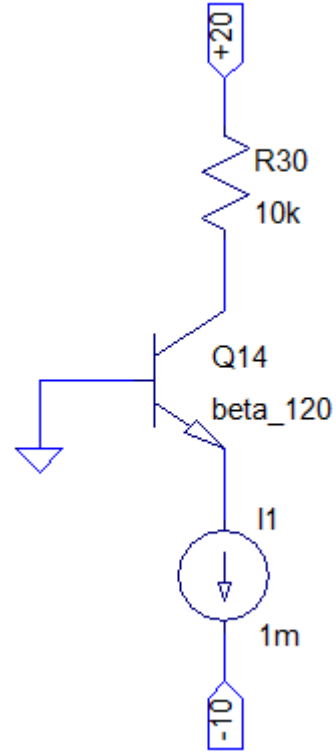

Q14
beta_120

I1
1m

R30
10k

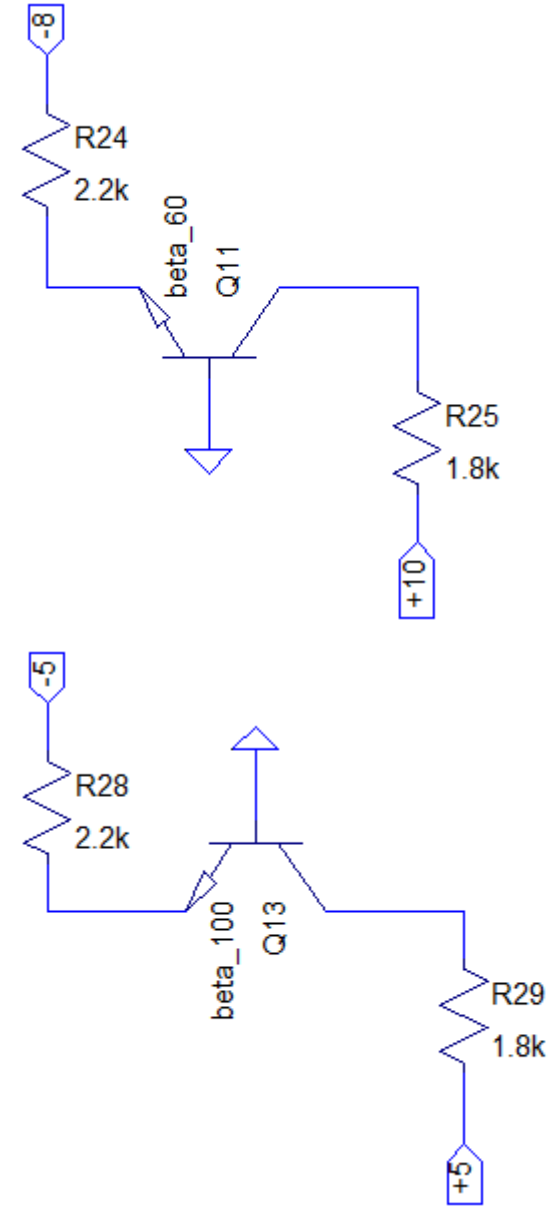


beta_60
Q11

R25
1.8k

beta_100
Q13

R28
2.2k

R29
1.8k

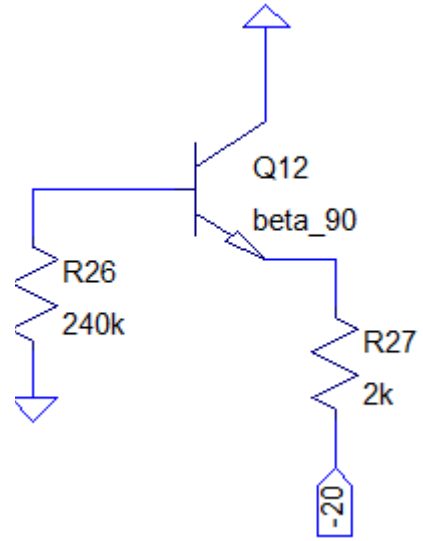

Q12
beta_90

R27
2k

R26
240k